

Introduction to Wire Antennas

Marc Tarplee, N4UFP
ARRL SC Section Manager



ARRL The national association for
AMATEUR RADIO

Part I

Introduction



ARRL The national association for
AMATEUR RADIO


What is an Antenna?

- **An antenna is a device that:**
 - Converts RF current applied to its feed point into electromagnetic radiation.
 - Intercepts energy from a passing electromagnetic wave, which appears as an RF voltage across the antenna's feed point.
- **Any object that can carry an electric current can act as an antenna.**




ARRL The national association for
AMATEUR RADIO

Transmitting Antenna

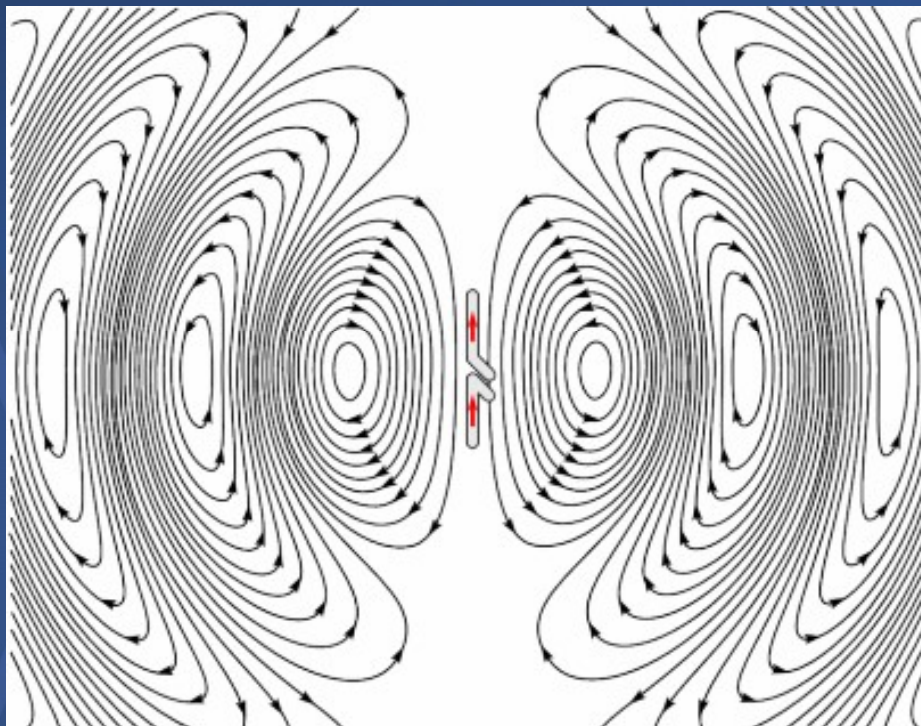


ARRL The national association for
AMATEUR RADIO

Receiving Antenna

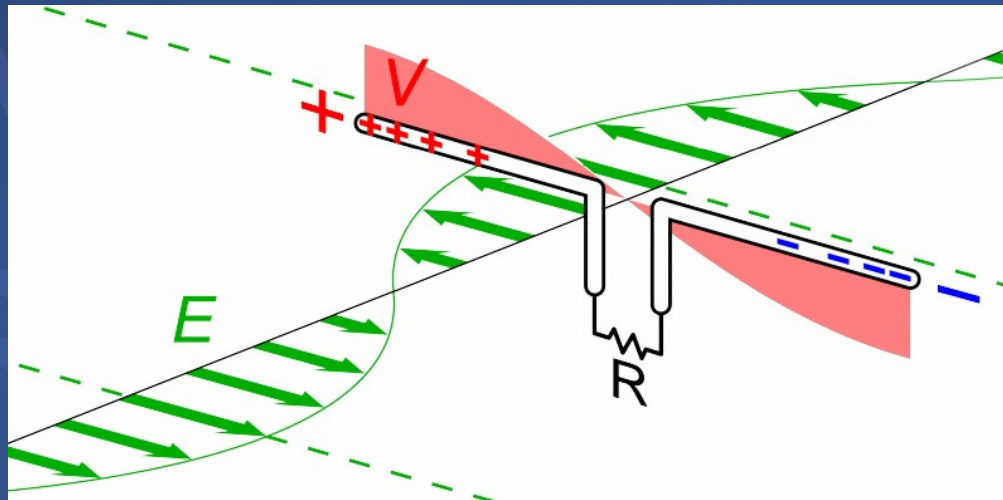

ARRL The national association for
AMATEUR RADIO

Types of Antennas

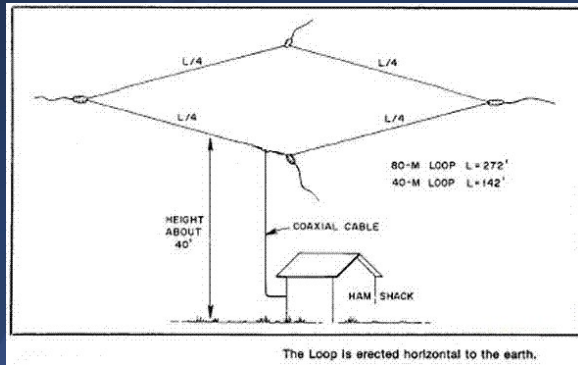

- There are some of the many types of antennas in use
- This presentation focuses on wire antennas



ARRL The national association for
AMATEUR RADIO

Basic Antenna Properties

- **Radiation Pattern**
 - Variation of antenna radiation with direction
 - Most common 2D patterns: azimuth (parallel to ground) and elevation (perpendicular to ground)
- **Directivity (Gain)**
 - Ratio of maximum radiation of an antenna under test to a reference antenna
- **Input Impedance**
 - Measured at the antenna's input – varies with frequency
- **Bandwidth**
 - Range frequencies over which SWR < 2.0
- **Reciprocity**
 - Antennas exhibit the same characteristics when receiving or transmitting



ARRL The national association for
AMATEUR RADIO

Part II

The Dipole



ARRL The national association for
AMATEUR RADIO

The Simplest Antenna

- A dipole antenna is created when we break a wire somewhere along its length and feed RF into it.
- A dipole's properties are determined by:
 - Relative length of the wire in wavelengths
 - Position of the feed point
 - Diameter of the wire
- This definition is very general, but there are some specific types of dipoles worth looking at more closely



ARRL The national association for
AMATEUR RADIO





The Half-Wave ($\lambda/2$) Dipole

- A dipole whose length is approximately $\lambda/2$ has some useful properties:
 - Its input impedance is generally between 30 and 80 ohms, so it can be fed directly with 50 or 75 ohm coaxial cable.
 - The physical length is manageable (between 16.5 and 133 feet on the HF bands)
 - It can be hung between two supports or from a single center support (inverted-vee)



ARRL The national association for
AMATEUR RADIO


$(\lambda/2)$ Dipole Properties

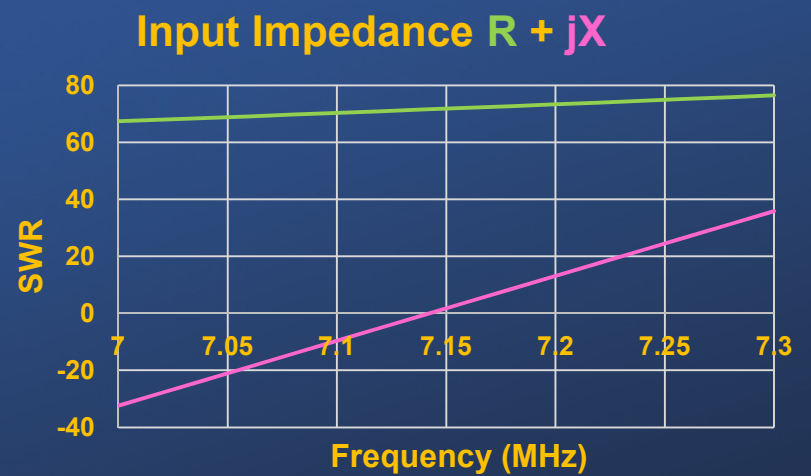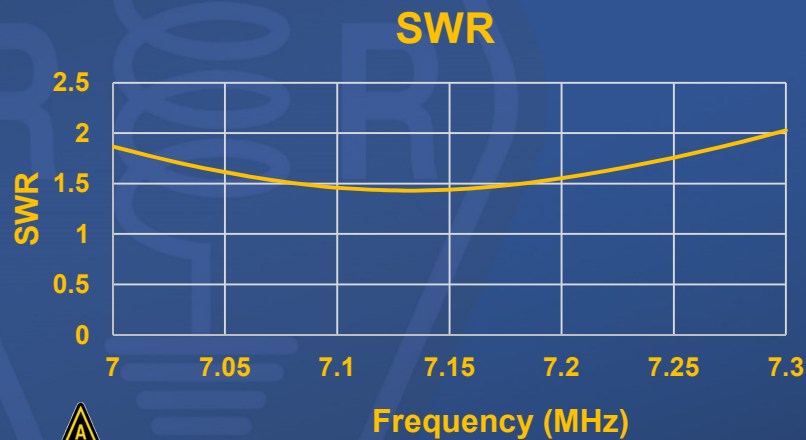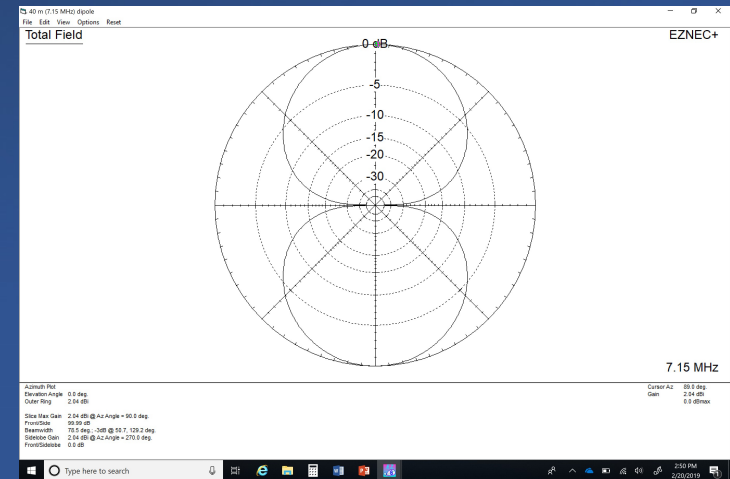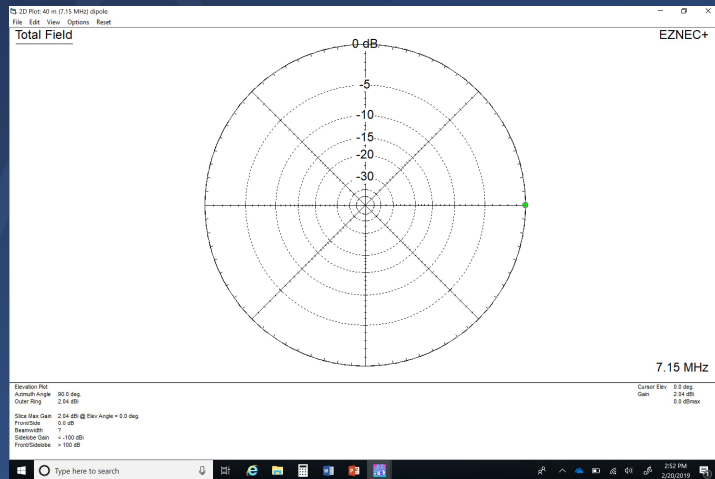

ARRL The national association for
AMATEUR RADIO

Design Table: $\lambda/2$ Dipole

BAND	LENGTH (#14 THHN WIRE)
160 (1.83 MHz)	255 ft 9 in
80 (3.8 MHz)	132 ft 2 in
40 (7.1 MHz)	65 ft 11 in
30	46 ft 3 in
20	33 ft 0 in
17	25 ft 10 in
15	22 ft 1 in
12	18 ft 9 in
10 (28.4 MHz)	16 ft 6 in

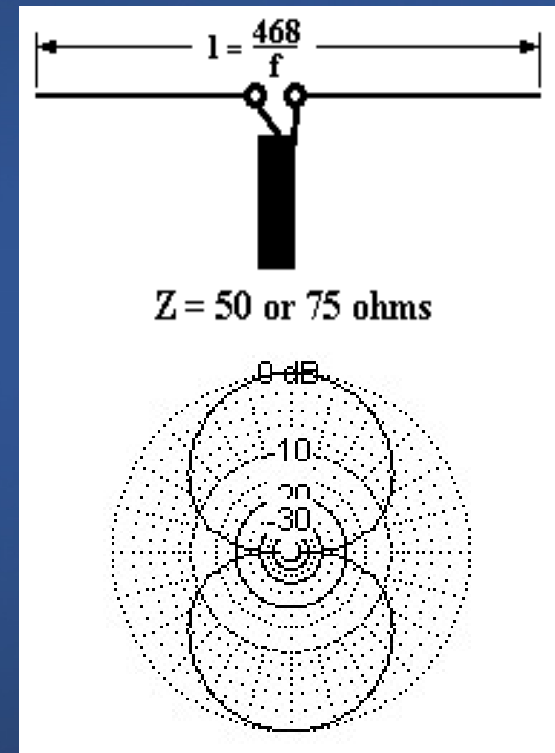

Variations on a Theme:

1λ , 1.28λ and $3\lambda/2$ Dipole

- 1λ dipole (2 half waves in phase)
 - Wire length is $\sim 0.95\lambda$
 - Input $Z \sim 5000\ \Omega$ – could be matched with $\lambda/4$ $450\ \Omega$ series section
 - Directivity = 1.5 dBd
- 1.28λ dipole
 - Provides maximum broadside gain from a single wire, ~ 3 dBd
 - Input $Z = 200 - j1000\ \Omega$ (can be matched with $3\lambda/16$ $450\ \Omega$ series section)
- $3\lambda/2$ dipole (original G5RV)
 - Provides some gain in several directions
 - Input $Z = 110\ \Omega$ (can be matched with $\lambda/4$ $75\ \Omega$ series section)



ARRL The national association for
AMATEUR RADIO


1λ, 1.28 λ and 3λ/2 Dipoles

•

1λ

1.28 λ

3λ/2

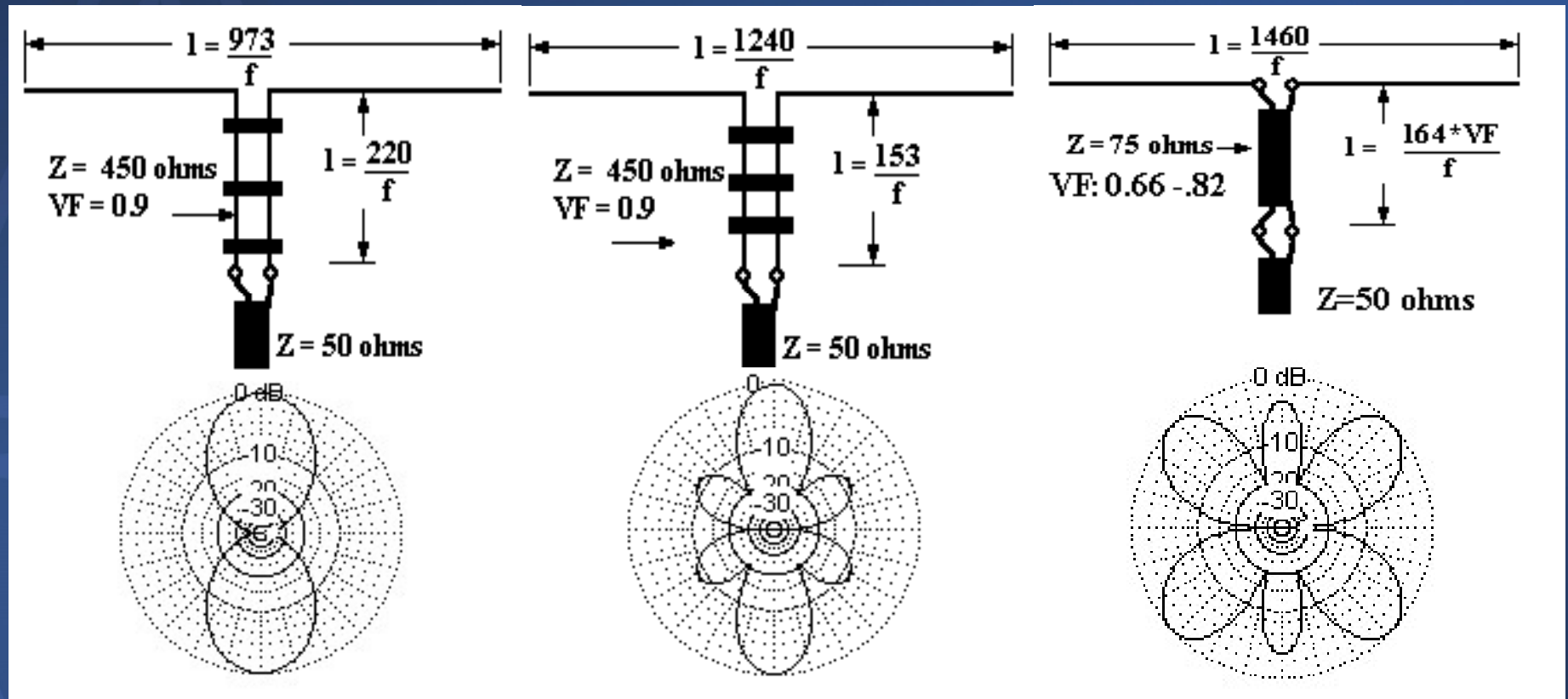

ARRL The national association for
AMATEUR RADIO

Design Table:


1 λ , 1.28 λ and 3 λ /2 Dipole

BAND	LENGTH (#14 THHN WIRE)		
	1 λ DIPOLE	1.28 λ DIPOLE	1.5 λ DIPOLE
160 (1.83 MHz)	517 ft 0 in	677 in 7 in	775 ft 6 in
80 (3.8 MHz)	248 ft 4 in	326 ft 4 in	372 ft 6 in
60	175 ft 2 in	224 ft 2 in	262 ft 9 in
40 (7.1 MHz)	132 ft 2 in	169 ft 2 in	198 ft 3 in
30	92 ft 10 in	118 ft 10 in	139 ft 3 in
20	66 ft 0 in	84 ft 6 in	99 ft 0 in
17	51 ft 8 in	66 ft 2 in	77 ft 6 in
15	44 ft 0 in	56 ft 4 in	66 ft 0 in
12	37 ft 6 in	48 ft 0 in	56 ft 3 in
10 (28.4 MHz)	33 ft 0 in	42 ft 5 in	49 ft 6 in

BAND	SERIES MATCHING SECTIONS		
	1 λ DIPOLE -450 Ω LINE	1.28 λ DIPOLE - 450 Ω LINE	1.5 λ DIPOLE - 75 Ω RG11
160 (1.83 MHz)	120 ft 3 in	83 ft 7 in	88 FT 9 IN
80 (3.8 MHz)	57 ft 11 in	40 ft 3 in	42 ft 9 in
60	41 ft 1 in	26 ft 7 in	30 ft 5 in
40 (7.1 MHz)	31 ft 0 in	21 ft 7 in	22 ft 11 in
30	21 ft 9 in	15 ft 1 in	16 ft 0 in
20	15 ft 6 in	10 ft 10 in	11 ft 6 in
17	12 ft 2 in	8 ft 6 in	9 ft 0 in
15	10 ft 4 in	7 ft 2 in	7 ft 8 in
12	8 ft 10 in	6 ft 2 in	6 ft 6 in
10 (28.4 MHz)	7 ft 9 in	5 ft 5 in	5 ft 9 in

The ZS6BKW Dipole

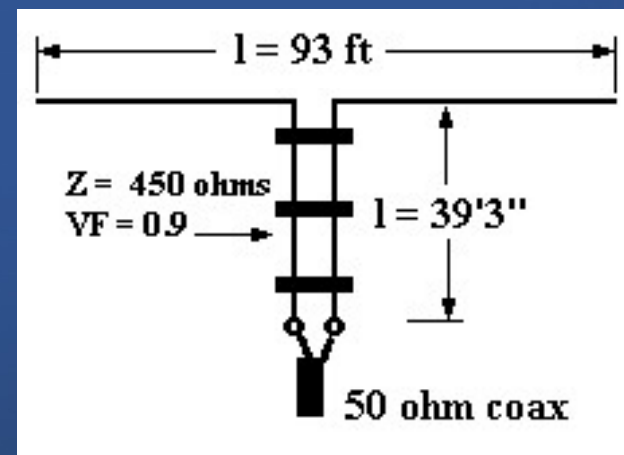- This antenna consists of ~93 ft of #14 THHN wire fed in the center through a 39ft 3in section of 450 Ω ladder line:
- This antenna is a good match ($\text{SWR} < 2.0$) to 50 Ω coax on the following bands: (other bands require a matching network)
 - Bottom 100 KHz of 80m
 - 40m
 - 20m
 - 17m
 - 12m
 - 10m
- If you can only put up one antenna, this is the one.



ARRL The national association for
AMATEUR RADIO

Part III


The Vertical Monopole (Marconi Antenna)



ARRL The national association for
AMATEUR RADIO

Reflections and Images

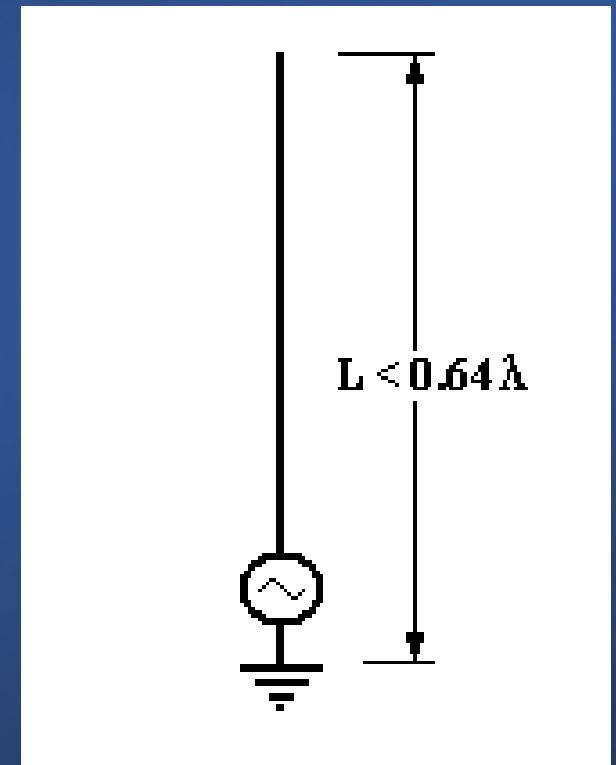- A vertical monopole (Marconi) antenna is a vertical wire fed against ground.
- The ground surrounding the antenna is very important - the monopole's image in the ground supplies the “missing half” of a vertical dipole
- RF reflections from the ground also greatly influence the antenna's impedance and radiation pattern



ARRL The national association for
AMATEUR RADIO

The Importance of a Good Ground

- The ground is part of the vertical antenna, not just a reflector of RF, unless the antenna is far removed from earth (usually only true in the VHF region)
- RF currents flow in the ground in the vicinity of a vertical antenna. The region of high current is near the feed point for verticals less than $\lambda / 4$ long, and is $\sim \lambda / 3$ out from the feed point for a $\lambda / 2$ vertical.
- To minimize losses, the conductivity of the ground in the high current zones must be very high.
- Ground conductivity can be improved by using a ground radial system, or by providing an artificial ground plane.
- Ground planes are most practical in the VHF range. At HF, radial systems are generally used.




ARRL The national association for
AMATEUR RADIO


Ground Radials

- Ground radials may be laid on the ground and should not be insulated from ground
- The radial wires should run radially out from the antenna feed point.
- The length of each radial is dependent on the number of radials
- In general, more short radials are preferable to a few long ones

Optimal Ground Radial Length

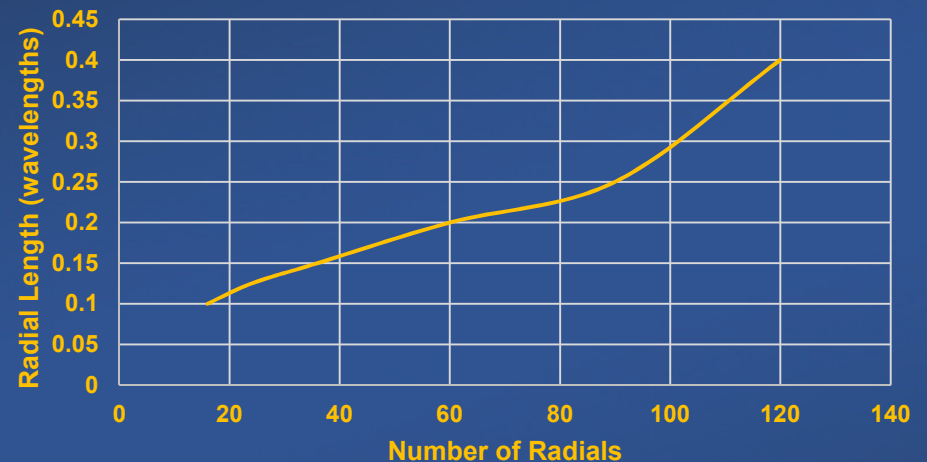


Ground Losses

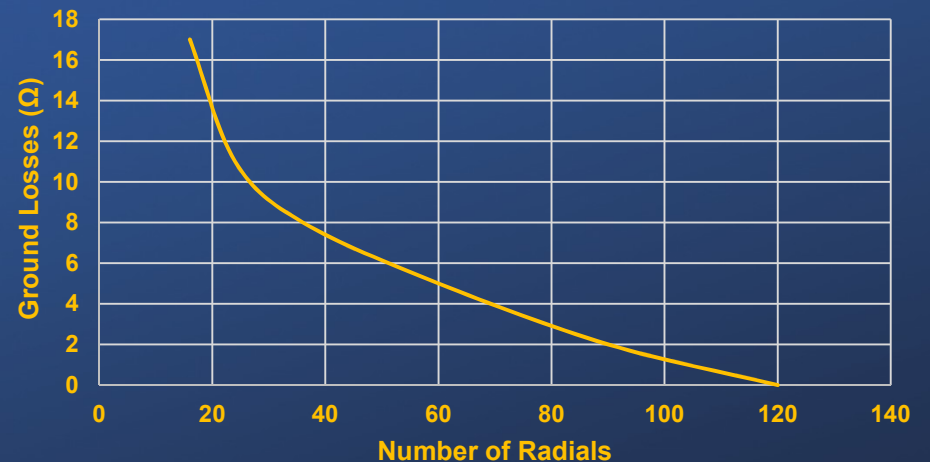

The Quarter-Wave ($\lambda/4$) Monopole


- The radiator is a vertical wire $\sim \lambda/4$ long
- Input $Z = Z_{ANT} + R_{GND} + R_{REF}$ (35-70 Ω)
- Efficiency $\eta = |Z_{ANT}| / |Z_{IN}|$ - often much less than 100%
- The big advantage of the $\lambda/4$ monopole is that it radiates better than a dipole at low angles (particularly on the lower bands)

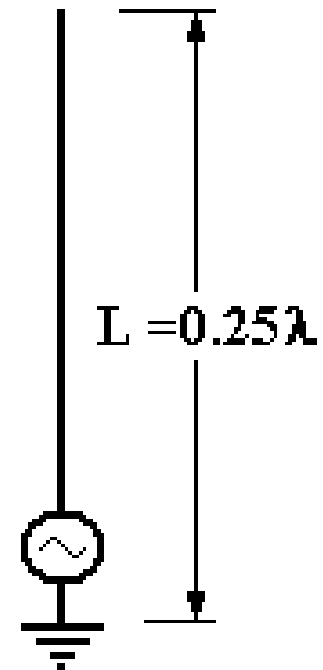

ARRL The national association for
AMATEUR RADIO

$\lambda/4$ Monopole Radiation Patterns

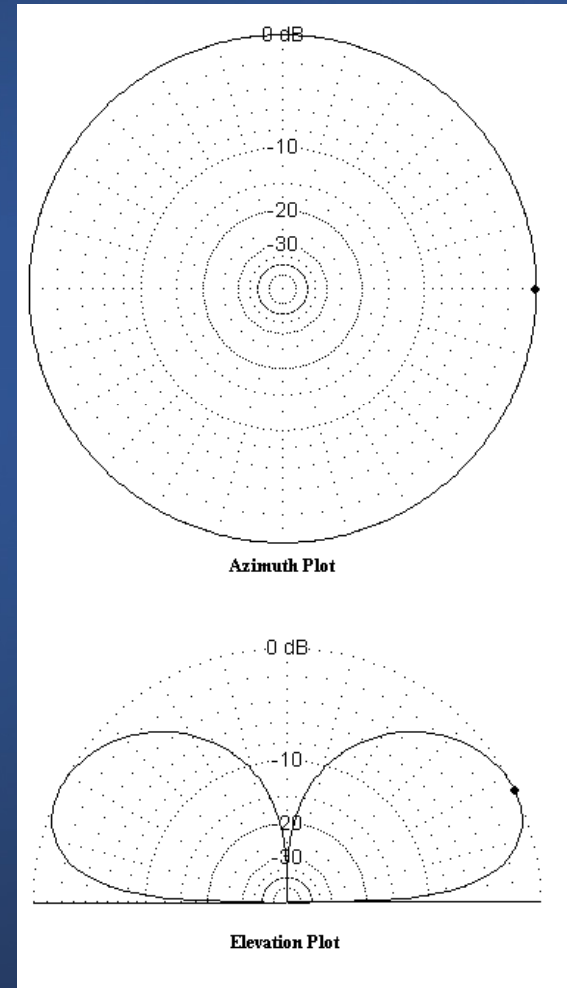- The antenna is omnidirectional in the horizontal plane
- Radiation in the vertical plane is concentrated at low angles
- Increasing ground conductivity decreases the angle of maximum radiation in the vertical plane



ARRL The national association for
AMATEUR RADIO

Design Table - $\lambda/4$ Monopole

BAND	RADIATOR LENGTH (#14 THHN)
160	127ft 10 in
80 (3.60 MHz)	65 ft 0 in
75 (3.90 MHz)	60 ft 0 in
60	43 ft 9 in
40 (7.1 MHz)	33 ft 0 in


- Data is only included for the low bands, because on the higher HF bands, in most cases, a horizontal wire antenna such as a dipole is a better choice.



ARRL The national association for
AMATEUR RADIO

The Inverted-L Monopole

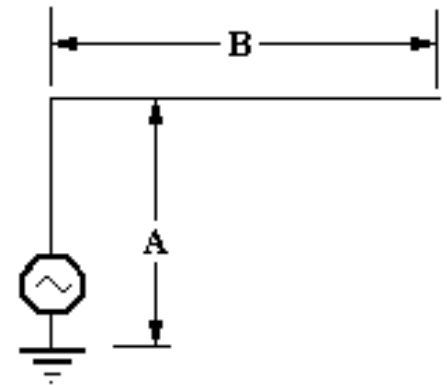- The radiator is a vertical wire that has been folded to fit available supports. Overall length $A+B \sim 0.3\lambda$
- Typically the vertical section is $\sim\lambda/8$
- $Z_{in} \sim 30\Omega - 75\Omega$
- Radiation patterns are similar to a $\lambda/4$ vertical, with a small amount of directivity in the horizontal pattern (typically less than 2 dB)



ARRL The national association for
AMATEUR RADIO

Design Table – Inverted-L

BAND	VERTICAL SECTION LENGTH	HORIZ. SECTION LENGTH
160	65 ft 9 in	77 ft 10 in
80 (3.60 MHz)	31 ft 11 in	37 ft 0 in

- Data is only included for the 160 and 80 meter bands, because the height required for a $\lambda/4$ vertical for the 60 and 40 meter bands is less and doesn't usually necessitate installation as an inverted-L



ARRL The national association for
AMATEUR RADIO

Part IV

Antenna Measurements



ARRL The national association for
AMATEUR RADIO

Characterizing Antenna Performance

- Ideally, we would like to know at least three things about an antenna:
 - Radiation Pattern
 - Input Impedance
 - Bandwidth
- Unfortunately, only one of these, bandwidth, is easy to measure



Making Antenna Performance Measurements

- Radiation patterns can be very useful, but are very difficult to measure. An antenna test range is required for accurate measurements.
- An impedance bridge or vector network analyzer (\$\$\$) is required for Input Z measurements
- Bandwidth can be easily be determined from SWR measurements.



ARRL The national association for
AMATEUR RADIO

SWR

- It turns out that SWR is the simplest, cheapest measurement we can make on an antenna system.
- SWR is the ratio of maximum to minimum voltage on a transmission line.
- Most amateur stations have equipment for measuring SWR.
- What do SWR measurements tell us?
 - The degree of mismatch between the antenna and feed line
 - The bandwidth of the antenna system
- As with any measurement, some interpretation is required to get useful interpretation from SWR data



ARRL The national association for
AMATEUR RADIO


SWR – Mathematical Relationships

- Max Voltage $V_{\max} = \sqrt{2PZ_0(SWR)}$

- Minimum Voltage $V_{\min} = \sqrt{\frac{2PZ_0}{(SWR)}}$

- Reflection Coefficient $|\rho| = \sqrt{\frac{P_R}{P_F}}$



- SWR $SWR = \frac{1 + |\rho|}{1 - |\rho|}$

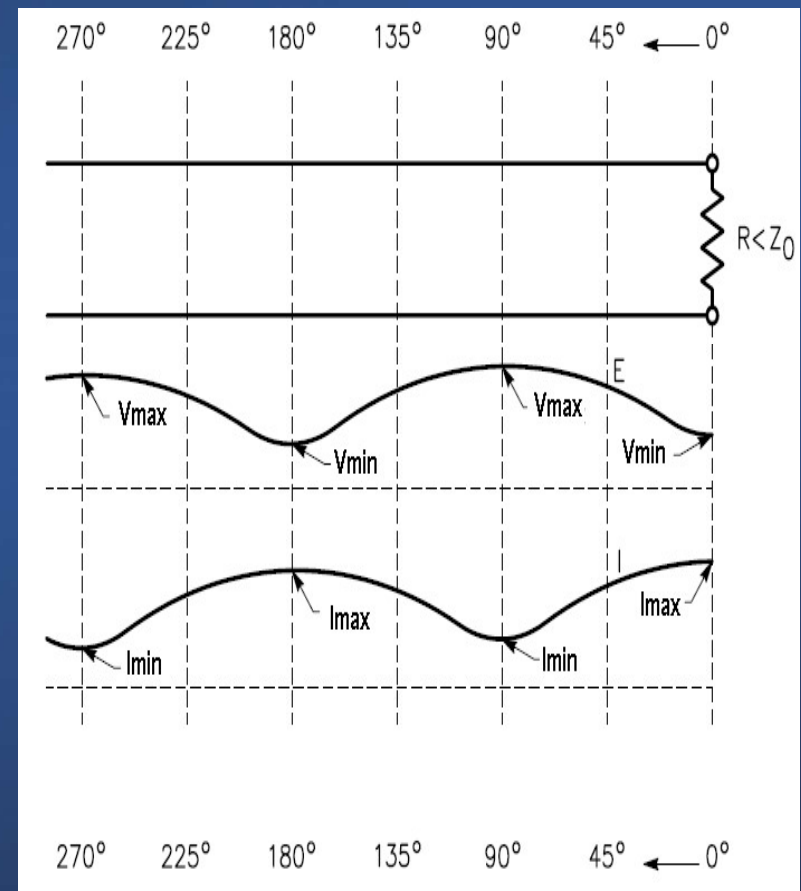

ARRL The national association for
AMATEUR RADIO

Measuring SWR

- Some transceivers have built in SWR meters. To measure SWR all one need do is look at the display
- An external SWR meter may also be used. There are two types:
 - Single needle unit – two step process
 - Meter sensitivity is adjusted to make meter read full scale on forward power setting.
 - In reverse power setting, SWR is read off meter scale
 - Crossed-Needle unit – one step process
 - SWR is indicated by point where forward and reverse power meter needles cross
- SWR is measured between the output of transmitter and the load (including matching networks)

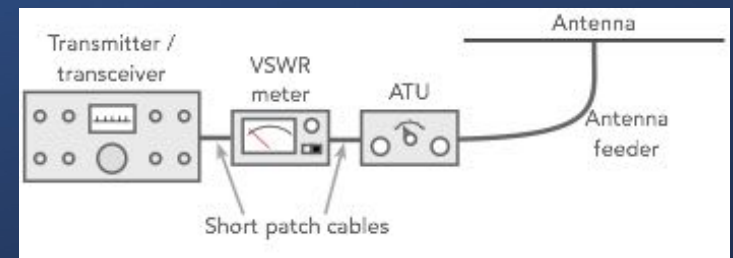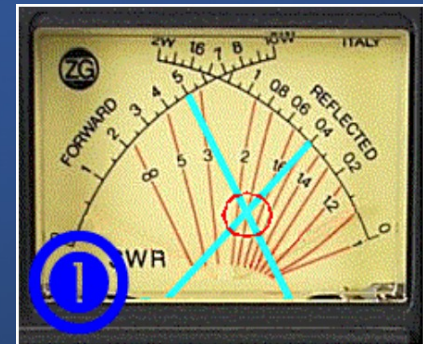

ARRL The national association for
AMATEUR RADIO

Power and SWR

- A power meter that can measure forward and reflected power may also be used to determine SWR.
 - Measure the forward power (P_F) and reverse power (P_R)
 - Use the following equation to compute SWR:

$$SWR = \frac{1 + \sqrt{\frac{P_R}{P_F}}}{1 - \sqrt{\frac{P_R}{P_F}}}$$

- Example: $P_F = 108W$ $P_R = 12W$

$$SWR = \frac{1 + \sqrt{\frac{P_R}{P_F}}}{1 - \sqrt{\frac{P_R}{P_F}}} = \frac{1 + \sqrt{\frac{12}{108}}}{1 - \sqrt{\frac{12}{108}}} = \frac{1 + \sqrt{.111}}{1 - \sqrt{.111}} = \frac{1 + .333}{1 - .333} = \frac{0.667}{0.333} = 2.0$$



ARRL The national association for
AMATEUR RADIO

Using an SWR meter to set up and antenna matchbox

- These instructions apply to modern matchboxes using a T-network.
 - Set the “TRANSMITTER” and “ANTENNA” controls to their midrange position
 - Measure the SWR.
 - While watching the SWR meter, set the “INDUCTANCE” control to the value that results in minimum SWR
 - Then adjust the “TRANSMITTER” and “ANTENNA” controls until the $SWR < 2.0$
 - If SWR cannot be reduced to less than 2.0, change the “INDUCTANCE” setting and try again.



ARRL The national association for
AMATEUR RADIO

Bandwidth and SWR

- Once the antenna and line are matched to the transmitter, one can use the SWR meter to determine the antenna system bandwidth.
 - Use the SWR meter to determine the lower frequency (F_L) at which $SWR = 2.0$
 - Use the SWR meter to determine the higher frequency (F_H) at which $SWR = 2.0$
 - The bandwidth can be computed using the following equation:

$$BW = F_H - F_L$$

- Example: $F_L = 3.64 \text{ MHz}$ $F_H = 3.78 \text{ MHz}$

$$BW = F_H - F_L = 3.78 - 3.64 = 0.14 \text{ MHz} = 140 \text{ KHz}$$



How important is SWR?

Is high SWR bad?

- The fact we measure high SWR for a particular antenna system, DOES NOT MEAN that the antenna is not radiating!! The antenna gets all the transmitter's power, less any line loss.
 - Example: we transmit a 1.8 MHz, 100W carrier into a short dipole antenna through 65 feet of RG-8 coax, whose loss is 0.17 dB. The SWR at the antenna is 19.0.
 - The forward power is 383W
 - The reflected power is 310 W
 - The power going into the antenna is 73W



ARRL The national association for
AMATEUR RADIO

SWR and Line Loss

- In the example on the last slide, we saw that 100 W transmitted into 65 feet of RG-8 connected to an antenna whose SWR = 19 resulted in 73 W reaching the antenna.
- If the SWR had been 1.0, 96W would have reached the antenna.
- Operating transmission lines under high SWR increases line loss!



ARRL The national association for
AMATEUR RADIO

SWR and Line Selection

- Because coaxial cable is relatively lossy, it should only be used in situations where $SWR < 3.0$ because:
 - Attenuation in coax rises quickly with increasing SWR
 - High voltages associated with high SWR may break down the dielectric
- In situations where the $SWR > 3.0$, use open-wire line or ladder line
 - It has much lower loss, even when the $SWR > 10.0$
 - Dielectric breakdown is much less likely



ARRL The national association for
AMATEUR RADIO

Is low SWR always good?

- Absolutely not!!
- Consider a dummy load.
 - It is designed to show $SWR = 1.0$ over a wide range of frequencies
 - It is designed NOT TO RADIATE
- Not convinced? Consider a mobile antenna used for 75 phone operation, whose $R_{IN} = 4$ ohms.
 - Poor installation – $Z_{LOAD} = R_{IN} + R_{GROUND} = 4\Omega + 50\Omega = 54\Omega$. $SWR = 1.1$ $\eta=7.4\%$
 - Good installation - $Z_{LOAD} = R_{IN} + R_{GROUND} = 4\Omega + 20\Omega = 24\Omega$. $SWR = 2.1$ $\eta=17\%$
 - The antenna with higher SWR is actually more than twice as efficient!



SWR Recap

- SWR is the ratio of maximum to minimum voltage on a transmission line.
- Possible values for SWR range from 1.0 (perfect match) to ∞ (perfect mismatch)
- Line losses increase with increasing SWR
- High SWR is not necessarily bad
- Low SWR is not necessarily good
- Coaxial cable is a good feed line choice when $\text{SWR} < 3$
- Open wire line is a good choice when $\text{SWR} > 3.0$
-



ARRL The national association for
AMATEUR RADIO

Questions and Comments

73

Marc N4UFP



ARRL The national association for
AMATEUR RADIO